

DIGITAL CONTROL

Without Programming

by David Caldwell

A dedicated digital controller with intuitive settings makes it quick and easy to close a loop around a power supply, heater, motor, lamp, or other device.

Closed-Loop Challenges

Closed-loop controllers make automatic adjustments to maintain constant output despite varying conditions. Examples include supply voltage, fluid temperature, motor speed, and light intensity. These parameters would shift over time and load without consistent

correction.

Microcontrollers executing firmware are replacing op-amps with feedback networks that used to perform closed-loop control. These digital implementations are versatile but time-consuming to program and control demands often exceed processor resources. Considerable expertise is required to properly design a system to avoid oscillations or sluggish responses. We naturally observe events in the time-domain while control analysis is typically done in the frequency-domain, which can be complex and confusing.

One solution to these challenges is an automated closed-loop controller configured by intuitive time-domain settings. CLOZD™ is a control chip developed by Flextek Electronics that is versatile and easy to use. Just select the desired timing configuration through pin settings and quickly close a loop around a power supply, motor drive, lamp, heater, fan, Peltier, valve, actuator, or amplifier.

Controller drive is automatically adjusted until the measured sensor signal matches the desired command, as shown in Figure 1. The Digital-Signal-Processing (DSP)

Figure 1. CLOZD loop controller system application.


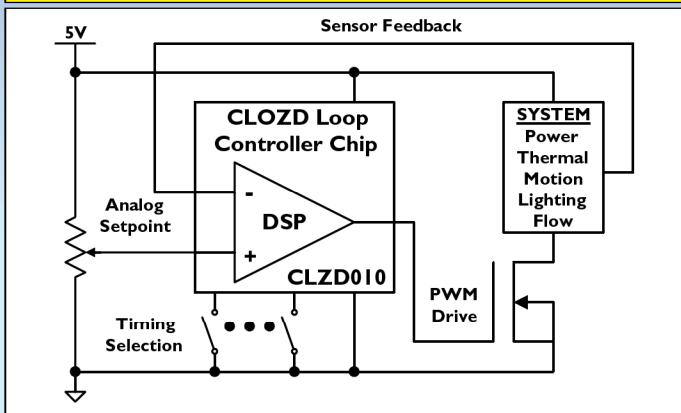


Figure 2. A thermal controller (for a 5W heater).
PWM = 488 Hz (PS=010, BIP=1) CLOZD = 134S (CS=0011, TIM=0).

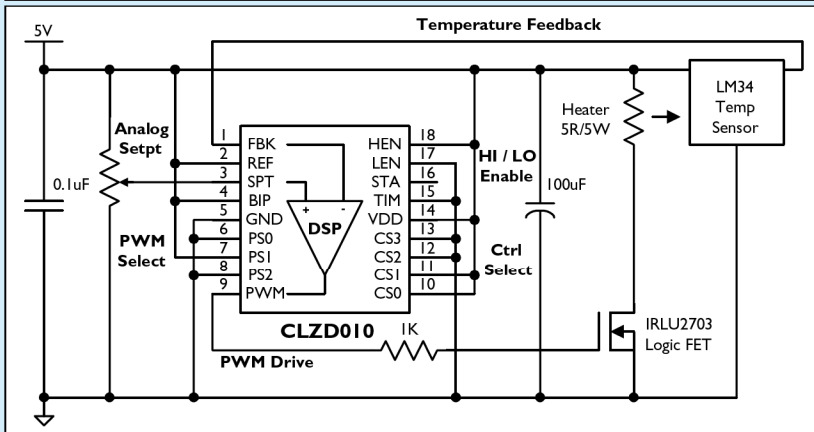

algorithms within the CLZD010 control chip compare the feedback sensor signal and the analog setpoint command to determine appropriate Pulse-Width-Modulator (PWM) drive for the plant. Typical plants include power, thermal, motion, lighting, and flow applications.

Thermal Controller

Thermal control systems are challenging because they have low level signals, long time constants, and multiple lag elements that can cause overshoot. However, the one shown in Figure 2 is quick and easy to configure for high performance with a few inexpensive parts. The duty cycle (percentage time

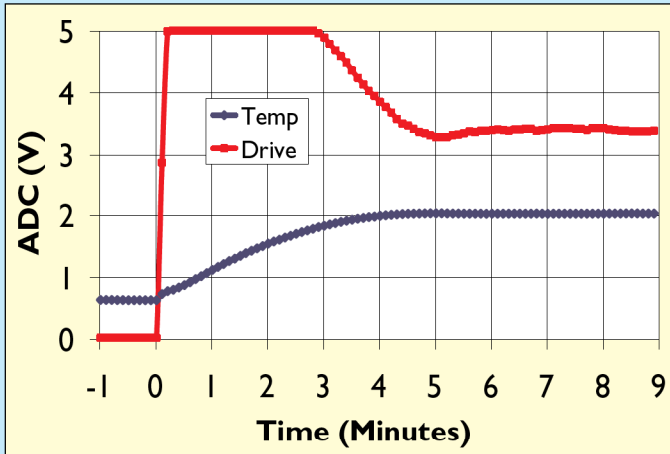



Figure 3. Temperature feedback and filtered PWM drive.

conducting) of the FET switch is adjusted until temperature feedback from the LM34 sensor is equal to the desired setpoint of the potentiometer. PWM frequency is set by the state of pins PS2-PS0 on CLZD010 while loop timing is set by pins CS3-CS0. Pins HEN and LEN are high and low enables.

The logic FET can be driven directly because low frequency PWM (PS2-PS0=488 Hz) is used with slow transitions (1K Ω gate resistor). Control timing was estimated by applying power to the heater and monitoring the temperature response. It took over 10 minutes for temperature to settle near its final value in an open-loop configuration. The temperature went from ambient to about two thirds of its final value in two to three minutes ($\tau = 1e^{-1} \approx 63\%$), so the timing of the system was set slightly faster (CS3-CS0=134 S).

Figure 3 shows the filtered (average) PWM drive and the temperature FBK response as a function of time. Notice that drive is high while the loop error (FPT-FBK) is large, but decreases prior to the temperature reaching its final value of 200°F (FBK=2 V) for fast response without overshoot.


Figure 4. A switching power amplifier (10V/10 A). PWM = 31.2 KHz (PS=110, BIP=0) CLOZD = 128 mS (CS=1110, TIM=1).

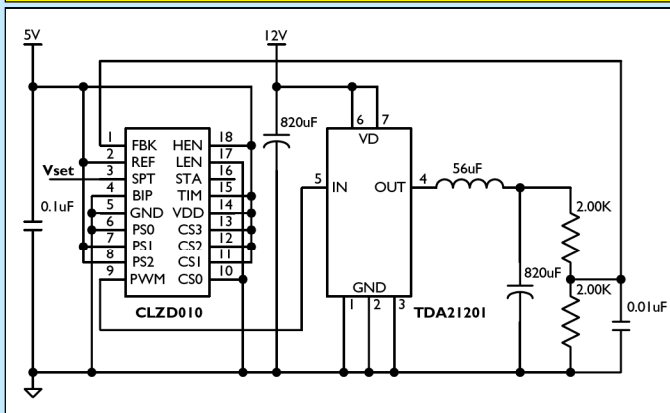

OCTOBER 2004

PROTEUS

The Complete Electronics Design System

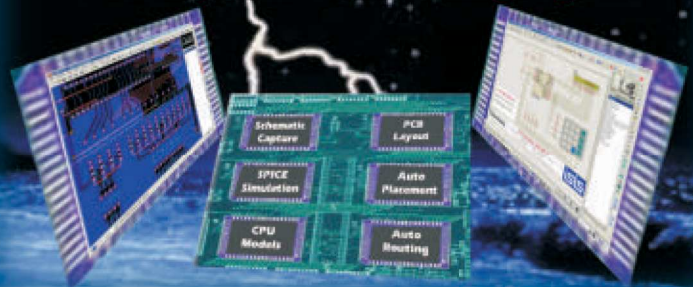

EASY TO USE CAD TOOLS

Schematic and PCB Layout

- Powerful and flexible schematic capture.
- Auto-component placement.
- Rip/entry PCB routing.
- Polygonal gridless ground planes.
- Library of over 8000 schematic and 1000 PCB foot prints.
- Bill of materials, DRC reports and more.

Mixed Mode SPICE Circuit Simulation

- Berkeley SPICE3F5 simulator with custom extensions for true mixed mode and interactive simulation.
- Six virtual instruments and 14 graph based analysis types.
- 6,000 models including TTL, CMOS and PLD digital parts.
- Fully compatible with manufacturers' SPICE models.

Proteus VSM - Co-simulation & debugging for popular Micro-Controllers

- Supports PIC16 & PIC12, AVR, 8051, HC11 and ARM micro-controllers.
- Co-simulate target firmware with your hardware design.
- Includes interactive peripheral models for LED and LCD displays, switches, keypads, virtual terminal and much, much more.
- Provides source level debugging for popular compilers and assemblers from HiTech PICC, Crownhill, IAR, Keil and others.

MicroChip PIC 18

- Supported models of the PIC 18 includes PIC18F242, PIC18F252, PIC18F442, PIC18F452, PIC18F248, PIC18F258, PIC18F448 and PIC18F458.

Basic Stamp BS1 and BS2

- Proteus VSM for BASIC Stamp contains everything you need to develop and simulate designs based around the BASIC Stamp.
- See examples in downloadable Demo at www.labcenter-electronics.com

"I finished my first design, schematic and PCB in one day."

"What a great tool! I love it."

DAN GILL

"For the cost of the software compared to the productivity gains, I consider Proteus to be pivotal in the commercial viability of my company and by far represents the best value for money of anything Tempus possesses."

ROB YOUNGS, Tempus Consulting

"PROTEUS stands out as the best all-round program in this review. Other programs reviewed have strengths in the pcb design process, Proteus maintains a constant high level of capability throughout. Whether a schematic, user-friendly interactive routing, configurable autoplacing, competent autorouting, or a combination of the above, PROTEUS handles everything very well." Electronic & Wireless World CAD Review Roundup

Save Time. Save Money.

Proteus Starter Kit - \$199 • Full System - \$1899

"This is clearly superior in every respect."

R4 SYSTEMS INC.

labcenter
Electronics

www.labcenter-electronics.com Tel: 905-898-0665 info@r4systems.com

Circle #55 on the Reader Service Card.

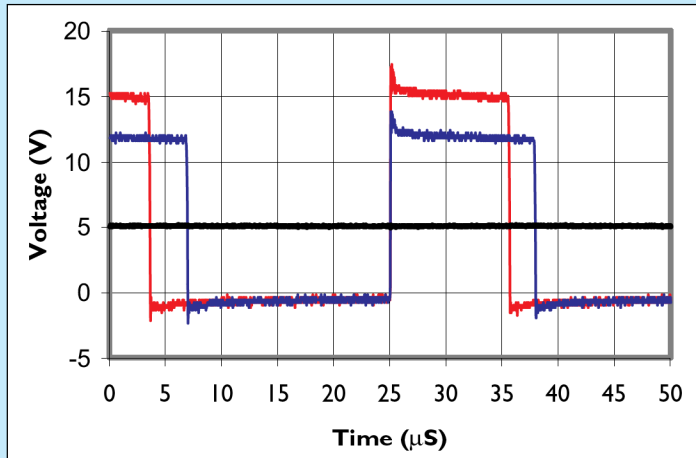


Figure 5. PWM drive waveforms for constant 5V output with 12V and 15V supplies.

Power Amplifier

Figure 4 illustrates a power amplifier that sources or sinks current while maintaining constant output voltage at twice $(1+2 K/2 K)$ the analog setpoint (V_{set}). This circuit is a switching converter that behaves like a low frequency (100 Hz) high power (10 V/5 A) op-amp. It requires few


parts that are inherently robust because critical functions are integrated, including digital signal processing, power switching, and thermal shutdown.

The half-bridge driver TDA21201 converts PWM logic levels to a high power pulse train that is averaged to a DC level by the output LC filter, as shown in Figure 5. The LC response is fast and susceptible to ringing, so high speed sampling and control calculations are required. For this reason, the 128 μ S control setting is used despite the 214 μ S time constant of the system ($\tau = LC^{1/2}$).


Figure 5 illustrates that more drive (higher duty cycle) is required at a lower supply voltage (12 V versus 15 V) to maintain constant output voltage.

Bidirectional Controller

Figure 6 illustrates a thermal controller that uses a Thermo-Electric-Cooler (TEC) or Peltier Cell to heat (PWM>50%) or cool (PWM<50%), depending on current direction through full-bridge driver LMD18201. This circuit is useful for applications requiring variable temperatures that include ambient. The full-bridge has two outputs that switch out-of-phase; one is low while the other is high. Both filtered outputs are equal at half the input voltage when



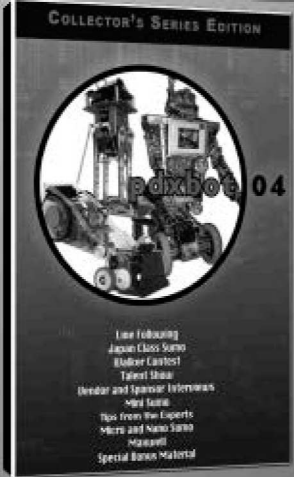THE PORTLAND AREA ROBOTICS SOCIETY,
PORTLAND STATE UNIVERSITY IEEE
ROBOTICS AND AUTOMATION SOCIETY AND
LEMON STUDIOS
PRESENT...
PDXBOT-04
...the DVD



COLLECTOR'S SERIES EDITION



PDXBOT-04

Line Following
Japan UDD Sumo
Rubber Carrots
Tallest Stack
Vendor and Sponsor Interviews
and More!
Tips from the Experts
Micro and Nano Samba
Playoffs
Special Bonus Material

This 2 hour long DVD was filmed at one of the West Coast's largest robotics exhibitions and contests. Brought to you from the Great Pacific Northwest, by the pioneers who brought the explosion of Sumo Robotics competition to the USA...

WATCH EVERY EXCITING MOMENT OF THE DAY'S EVENTS PLUS...

- Contest rules and insider hints for building competitive robots
- Backstage interviews with Vendors, Sponsors, Competitors, Sumo Pioneers and Much More!
- Bonus extras including new product release info and links to all products and companies mentioned in the DVD





Robotics & Automation Society

WWW.LEMONSTUDIOS.COM

YOUR TARGET FOR prototype circuit boards

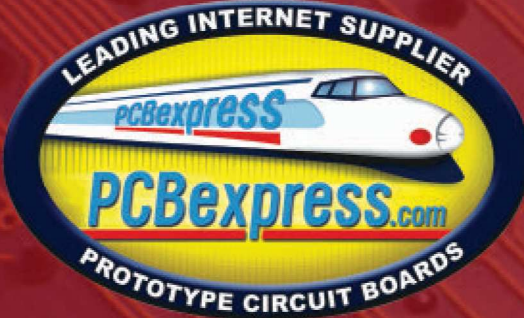Fast delivery - Great prices
Quality focused



LEADING INTERNET SUPPLIER

PCBexpress.com

PROTOTYPE CIRCUIT BOARDS

Easy order process
Immediate online pricing
Online walk-through tutorial
Fast! Turn around in less than 24hrs
High quality 2-6 layer pcbs up to 25pcs
No sign up or password needed to order
Real-time order status tracking
Boards routed to any shape
Live online support

Successfully selling online since 1997.
Experience you can trust! Try us out today at:
www.PCBexpress.com/nv

PWM=50%, so no power passes through the TEC. By tying the bipolar BIP pin of the controller high, the PWM initializes at 50% duty cycle rather than the usual 0%.

PC USB Control

Two chips under \$10.00 — each with free software drivers — enable the PC-based controller in Figure 7. The USB to serial converter provides the PC interface to the FlexController™ System-On-Chip (SOC), which commands setpoint and records system response through Visual Basic, while real-time control is performed by the CLOZD chip.

The FT232BM chip includes the hardware and PC drivers to communicate with microcontrollers through a USB port. The FCIC010 FlexController SOC combines the peripherals of a microcontroller with the ease of Visual Basic (or C++) programming through FTview™ Active X Control. These devices save valuable time by eliminating tedious low level programming and enabling customization through intuitive graphical development software.

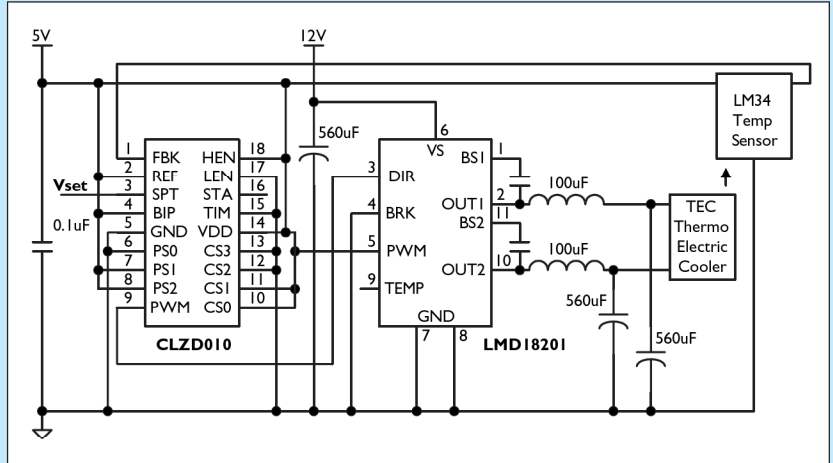


Figure 6. A bipolar thermo-electric cooler (12 V/3 A Peltier cell).
PWM = 31.2 KHz (PS=110, BIP=1) CLOZD = 134 S (CS=0011, TIM=0).

Visual Basic code for control from PC USB:

```
Private Sub FTview1_NewData()  
    FTview1.PWMduty = Setpoint           ' Write duty cycle  
    Feedback = FTview1.AD0volt          ' Read AD0 voltage  
    Write #1, Time, Setpoint, Feedback   ' Save data to File  
    FTview1.UpdateCmd = True            ' Update Control SOC  
End Sub
```

Surplus Sales of Nebraska

Fujitsu Stylistic 1000 Pen Computer

(EQP) FMW2430M

These are a real find!! Equipped with a 100 MHz AMD486 DX4 Processor. The display is Transmissive Monochrome and yields the highest resolution.



This style screen is back-lit for indoor use only. Sunlight will wash out display. Bare bones: These computers are Brand New, Never Used but include NO accessories. No battery, stylus pen, OS software, mouse or keyboard.

\$49 each

Volt-Pac Variac - 18 Amps / 0-140v

(TV) 9T92A28

State-of-the-art "Volt-Pac" designed General Electric variac delivers 18 amps @ 140 vac with 120 vac, 50/60 Hz input.



Frame 75.6" maximum diameter, 4-1/2" high. Reversible shaft allows bench mount as pictured, or panel mount. New in the box includes dial plate and knob.

\$219 each

NVidia Graphics Card Cooling Fan

(FAN) M THERM-1027B

NVidia graphics card cooling fan fits NVidia VisionTek. 3.26 cfm, 12 vdc, .09 amps. 2 pin connector.



Dimensions: 68mm x 60mm x 10mm high.

Manufactured by Millennium. 26,000 available!!

\$5 each - \$3.75 (12+), \$3.25 (100+), \$2.75 (1000+)

Please visit our website with over 2,000 pages and 10,000 images • www.surplussales.com



HI Manuals: 1,000s of radio, military and test equipment manuals on hand!!



Power Supplies: Low Voltage, High Voltage, Lighting, Precision.



High Impact Shipping Containers



Heatsinks: All Sizes and Shapes. Large Quantities for Manufacturers



Variacs: From 3 amps to 245 amps.



Transformers: High & Low voltage, chokes.



Knobs: of all types. Crank, 1/4", 1/8", dual sets, pointer, etc.



Collins Parts: For Amateur and Military.



Split Beads: For are all of your interference problems.



Shock Mounts



Vacuum Tubes: Over 1,000,000 vacuum tubes in stock!!



Toroids: Powdered Iron, Ferrite, Rods, Pot and E Cores



Fingerstock: Over 20 styles and sizes



Projector Lamps: Incandescent, quartz, tungsten halogen.



Rotary Switches: Ceramic, phenolic.

1502 Jones Street, Omaha, NE 68102 • Fax: 402-346-2939 • e-mail: grinnell@surplussales.com • Visa, Mastercard, American Express or Discover
Call or e-mail for shipping and total charges. All SPECIALS in this Ad only good for 30 day advertising cycle. No exceptions please.

Visit our website @ www.surplussales.com **800-244-4567** • **402-346-4750**

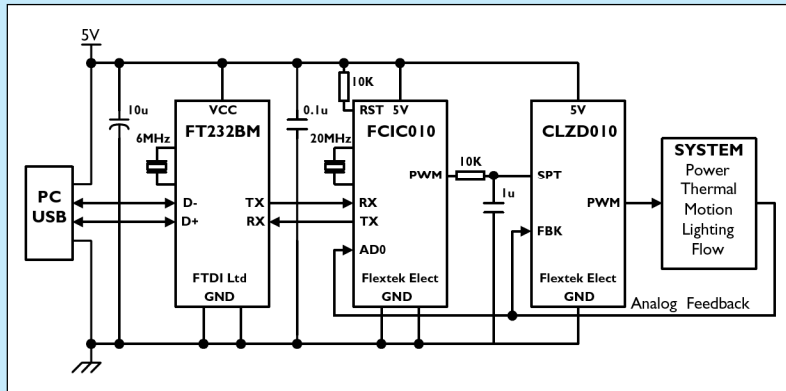


Figure 7. Closed-loop controller with PC USB interface.

familiar technology, and increased reliability by using proven components.

CLOZD Loop Controller utilizes advanced DSP techniques and algorithms to satisfy challenging real time control applications quickly and easily. Other methods and products require extensive programming and complex frequency-domain analysis. Configure the controller for a broad range of power, thermal, motion, lighting, and flow applications by selecting appropriate pin settings.

The CLSD010 control chip may be purchased for \$5.95 with complete data sheet and application notes from www.flex-tek.com Other components referenced in this article may be purchased from

www.digi-key.com, except the Peltier, which is available from www.allelectronics.com **NV**

Automated Control Advantages

Closed loop control may be the most common and, yet, the most challenging task in electronics. By automating this task with versatile interfaces that are easy to use, a wide range of custom applications are quickly satisfied. Users save time and money by quickly configuring the same components for multiple applications. This allows savings on parts by purchasing in volume, reduced development time by reapplying

About the Author

David Caldwell is the founder of Flextek Electronics, and has authored over a dozen papers and articles on power and control. You can reach him at djcaldwell@flex-tek.com

Turn Your Interest Into Income!

Get a Good Paying Job in Industrial Electronics
...We Train You at Home in Your Spare Time

Turn your hobby into a career you enjoy! A high-demand career that offers a stable future and pays top dollar. No night school, no travel. You do it at home using our government approved distance learning system. Includes one-on-one consultations, valuable International Society of Certified Electronics Technicians training, bench skills, professional instruments you keep and use on the job. Check us out!



- Industrial Robotics
- Numerical Control Machine Tools
- Computer Integrated Manufacturing Systems
- Process Controls
- Flexible Manufacturing Systems


For FREE Brochure

Call Toll-Free
1.800.658.1180
or visit www.aiilearn.com

or Mail Coupon
Atlantic International Institute
Department 1-045
2725 College Street
Jacksonville, FL 32205

If using coupon, please print all information clearly.
Name _____
Address _____
City _____ State _____ Zip _____

RF MODULES

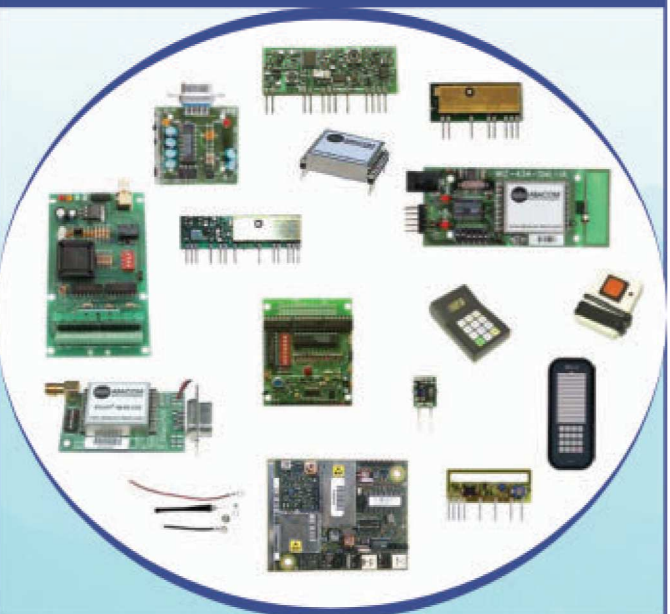

WWW.ABACOM-TECH.COM



Tel: +1(416)236 3858
Fax: +1(416)236 8866

abacom@abacom-tech.com